



# Industrial & Domestic Controls


Components for

- Smart Home Systems & Industrial Field Buses
- Power Supplies & Protection
- Sensors & Actuators
- Temperature Control
- Motor Soft Start
- Relay Drives
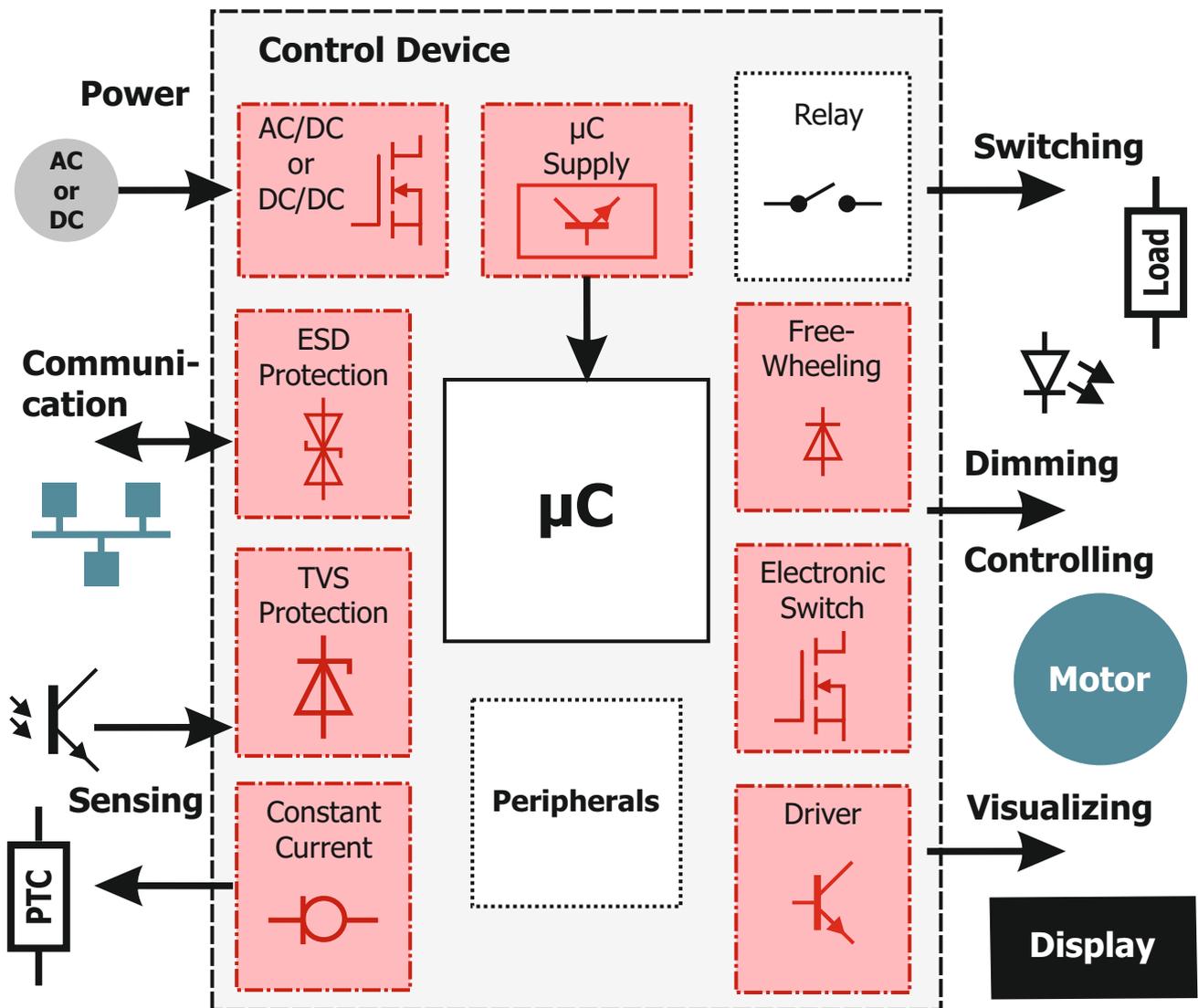
## Block Diagram


The heart of any industrial or domestic control device is either a microcontroller, a PLC (Programmable Logic Controller) or an IPC (Industrial PC). It handles the data processing, logic control, and interfacing. The latter includes digital inputs and outputs for status and PWM signals, switches or relays. Analog inputs measure variables such as temperature, brightness or frequency, while the outputs provide signal voltages or currents. Communication with other devices works via special interfaces such as Profibus, Profinet, EtherNet/IP, CANopen, Modbus or KNX. The power supply runs on typical input voltages of 24 V<sub>DC</sub>, 48 V<sub>DC</sub> or 110/230 V<sub>AC</sub>; sometimes, communication data are transferred via the power line itself.

Diotec provides dedicated semiconductor components acting between the microcomputer device and its surrounding, shown in the red marked blocks below.


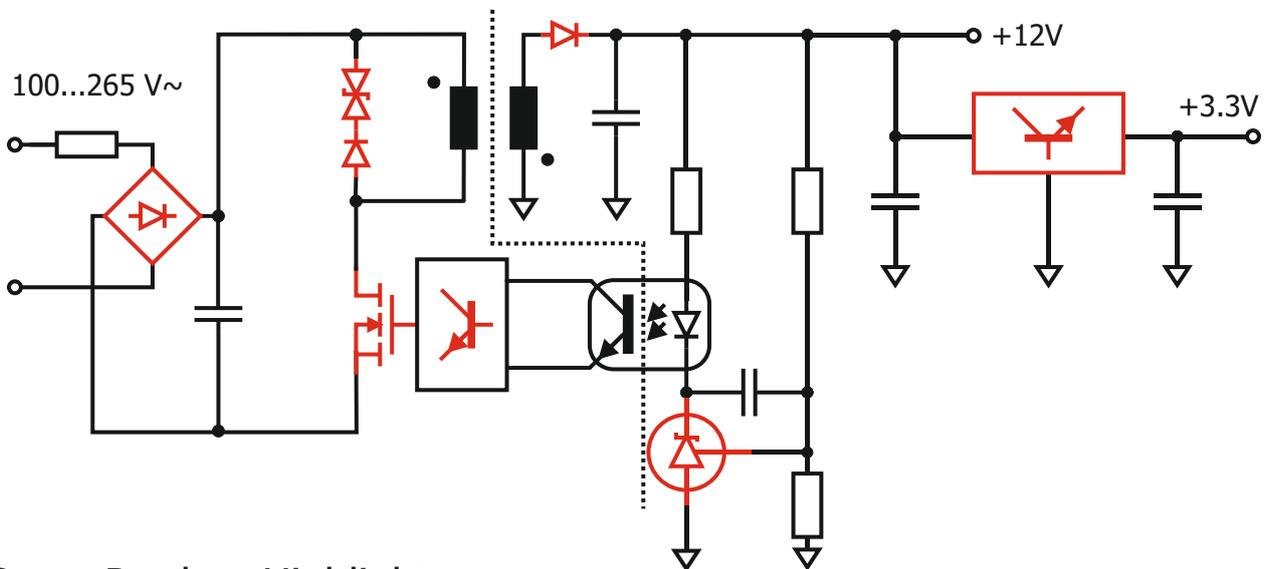
## 1. Universal Power Supply on 100...265 V AC Mains

A flyback converter is state of the art when it comes to wide range input AC to DC power supplies. Low power devices at fixed AC inputs could be supplied by simple capacitive circuits using a Zener for stabilization. Common to all of these is the fact that board space is rather restricted, calling for small size SMD components.




### Some Product Highlights

- MYS380** **Rectifier Bridge** 0.5 A / 800 V measuring 3x3 [mm]  
More see <https://diotec.com/en/productlist/B1.html>
- ABS15Y** **Rectifier Bridge** 1.5 A / 2000 V with 4 mm pitch  
More see <https://diotec.com/en/productlist/B1.html>
- TGL200CU10** **Snubber** 200 V TVS + 1000 V Blocking Diode in single MELF package  
More see <https://diotec.com/en/productlist/TVS.html>
- DI001N65PTK** **N-MOSFET** 1 A / 650 V with protected Gate in QFN3x3  
More see <https://diotec.com/en/productlist/FET.html>
- BC817BPN** **Dual NPN + PNP BJT** 45 V / 1 Apk in single SOT-26  
More see <https://diotec.com/en/productlist/T.html>
- SKL36** **Schottky** 3 A / 60 V in SOD-123FL  
More see <https://diotec.com/en/productlist/SBD.html>
- MMTL431A** **Shunt Regulator** 2.495 V ± 0.5 % in SOT-23  
More see <https://diotec.com/en/productlist/SHUNT.html>
- LDI8119-3.3EN** **LDO** 3.3 V / 0.5 A with Enable in SOT-23-5  
More see <https://diotec.com/en/productlist/VR.html>

## 2. Simple Capacitive Power Supply

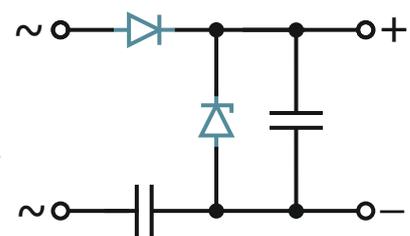
### Some Product Highlights

- S1Y** **Rectifier** 1 A / 2000 V in DO-214AC / SMA  
More see <https://diotec.com/en/productlist/R.html>
- AM2000** **Avalanche Rectifier** 1 A / 1600 V in DO-213AB / Melf  
More see <https://diotec.com/en/productlist/R.html>
- Z1SMA12** **Zener** 12 V / 1.5 W in DO-214AC / SMA  
More see <https://diotec.com/en/productlist/Z.html>


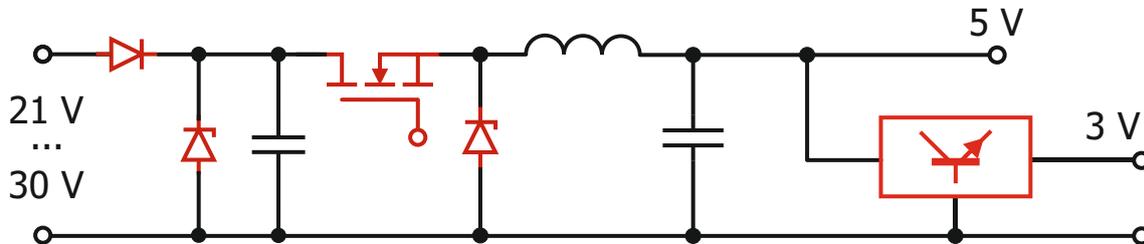
### 3. Power Supplies for Smart Home Systems (e. g. KNX) & Industrial Field Buses (e. g. PROFINET)

Both of this bus systems operate typically on 24 V DC. Internal circuits operate on a 5 V system, and 3 V is the supply for the  $\mu$ Controller. Board space saving is must and smallest SMD outlines are required.




#### Some Product Highlights

- SDB160WS**     **Polarity Protection Schottky** 1 A / 60 V in SOD-323P  
More see <https://diotec.com/en/productlist/SBD.html>
- SMF40A**     **TVS** 40 V / 200 W in SOD-123FL  
More see <https://diotec.com/en/productlist/TVS.html>
- DIOA35N06PGK**     **N-MOSFET** 0.35 A / 60 V with protected Gate in DFN1006  
More see <https://diotec.com/en/productlist/FET.html>
- SDB0530WT**     **Buck Diode Schottky** 0.5 A / 30 V in SOD-523  
More see <https://diotec.com/en/productlist/SBD.html>
- LDI734C3.0ENG**     **Capacitor-free LDO** 3.0 V / 0.3 A with Enable in QFN1x1  
More see <https://diotec.com/en/productlist/VR.html>
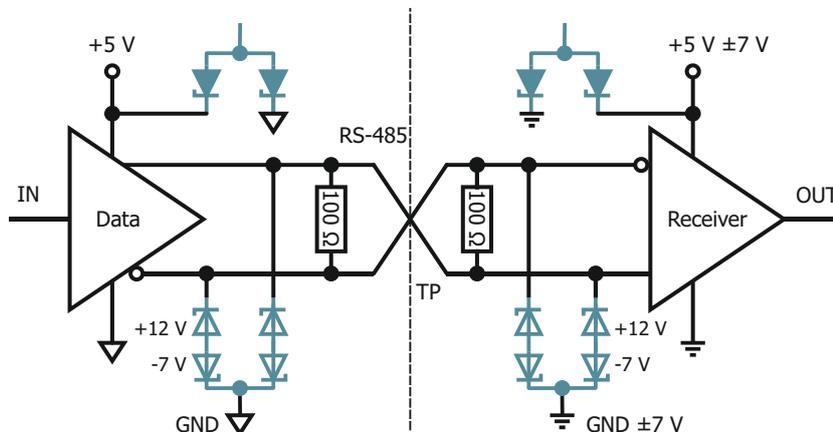
### 4. Protection of a RS-485 Field Bus

The RS-485 standard allows for a voltage shift of up to  $\pm 7$  V between different ground levels. As such the line voltage might differ from -7 V (0 V - 7 V) to +12 V (5 V + 7 V). The ESDB712 addresses this asymmetric voltage levels by offering a negative stand-off voltage of -7 V and a positive one of +12 V. The dual device protects both lines (Twisted Pair) of an RS-485 bus system. The ESD5V0CA protects against spikes on supply voltage..




#### Some Product Highlights

- ESD5V0CA**     **Dual ESD Protection** 2x 5.0 V /  $\pm 30$  kV in SOT-23  
More see <https://diotec.com/en/productlist/ESD.html>
- ESDB712**     **Asymmetric ESD Protection** +12 V / - 7 V /  $\pm 30$  kV in SOT-23  
More see <https://diotec.com/en/productlist/ESD.html>
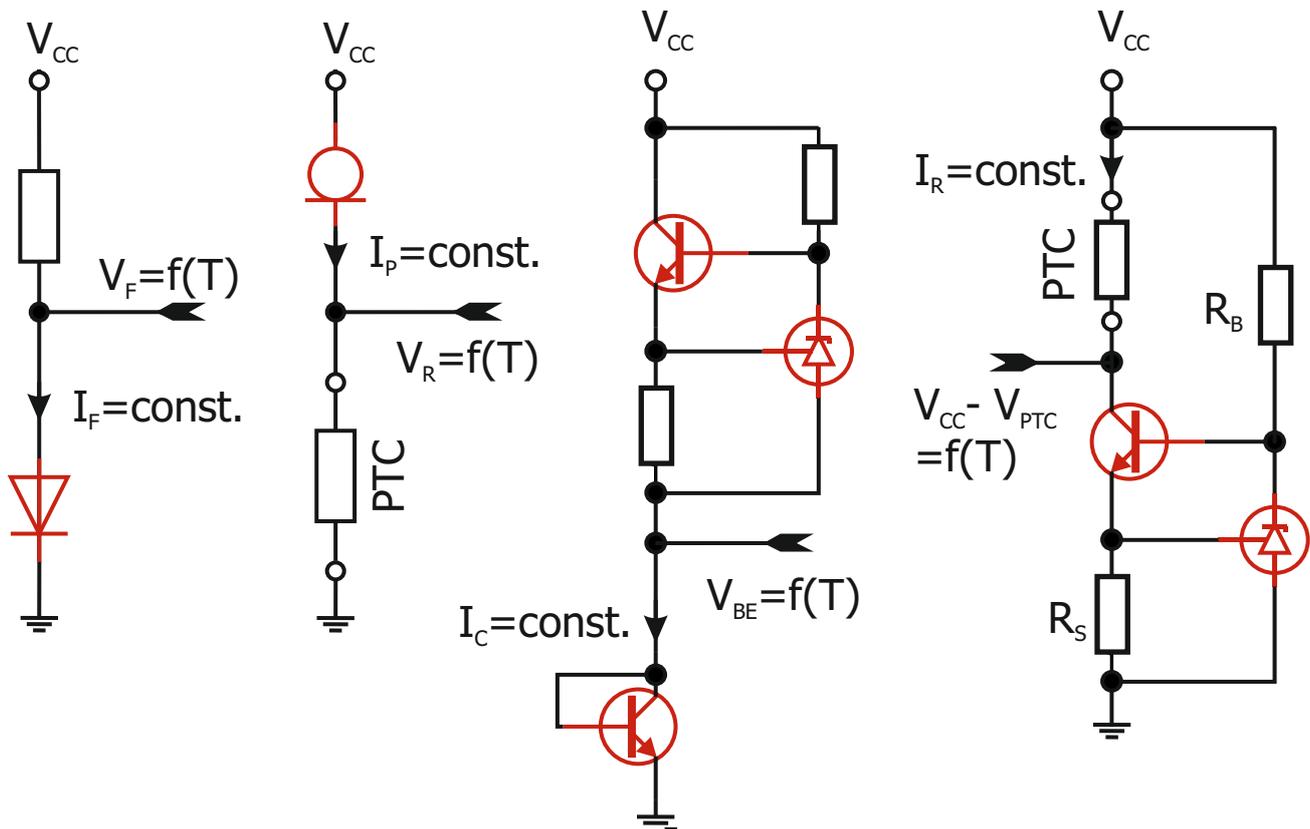
## 5. Temperature Sensing

If just a simple and rough temperature is required, one could use a diode out of the 4448 series (having a defined tight  $V_F$  range). Alternatively, a CLD (constant current regulator) along with an external PTC could do the job. For more accurate measurements, constant current circuits using a shunt regulator are the preferred option.




### Some Product Highlights

- 1N4448HP** **Small Signal Diode** 250 mA / 100 V in DFN1006-2  
More see <https://diotec.com/en/productlist/D.html>
- CL05M6F** **CLD** 5 mA / 190 V in SOD-123FL  
More see <https://diotec.com/en/productlist/C.html>
- BC846S** **Dual BJT** 100 mA / 65 V in SOT-363  
More see <https://diotec.com/en/productlist/T.html>
- MMTL431A** **Shunt Regulator** 100 mA / 36 V in SOT-23  
More see <https://diotec.com/en/productlist/SHUNT.html>
- BC846BP** **BJT** 100 mA / 65 V in DFN1006-3  
More see <https://diotec.com/en/productlist/T.html>
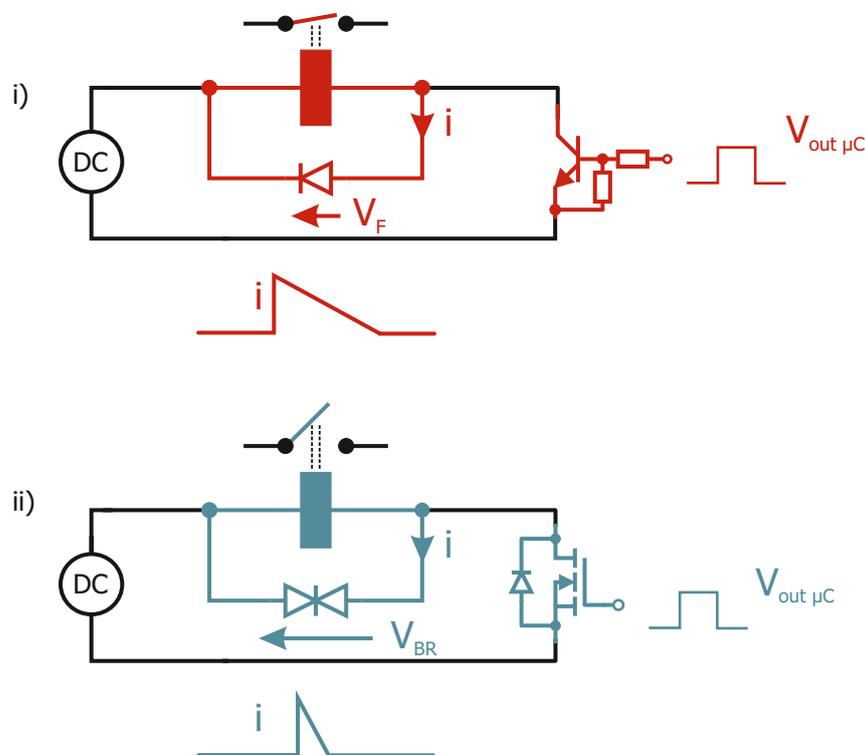
## 6. Driving and Free-Wheeling of Relay Coils

Relays offer the advantage of full galvanic isolation between logic levels of the control and high voltage mains. The relay coil requires a free-wheeling diode, in order to avoid voltage peaks when drive is turned-off. A simple diode can be used, but the counter-voltage to demagnetize the coil inductance is then just the diode's forward voltage drop, see figure i). A much faster demagnetization can be achieved by using the breakdown voltage of a bidirectional TVS, as shown in figure ii).

The relay can be driven by either a digital transistor or a logic level MOSFET. Both offer the advantage to be switched directly from a digital output of the micro-controller. Either device can be used together with a diode or TVS, there is no preference as the below figures might pretend.




### Some Product Highlights

<b>SRL1J</b>	<b>Standard Diode</b> 1A / 600 V in PowerSOD-323/DO-219AD More see <a href="https://diotec.com/en/productlist/R.html">https://diotec.com/en/productlist/R.html</a>
<b>MMDTA141DW</b>	<b>Dual Digital PNP Transistor</b> -100 mA / -50 V in SOT-363 More see <a href="https://diotec.com/en/productlist/DT.html">https://diotec.com/en/productlist/DT.html</a>
<b>MMDTC124EE</b>	<b>Digital NPN Transistor</b> 30 mA / 50 V in SOT-523 More see <a href="https://diotec.com/en/productlist/DT.html">https://diotec.com/en/productlist/DT.html</a>
<b>TGL34-33CA</b>	<b>Bidirectional TVS</b> 33 V / 150 W in DO-213AA/MiniMelf More see <a href="https://diotec.com/en/productlist/TVS.html">https://diotec.com/en/productlist/TVS.html</a>
<b>SMF12CA</b>	<b>Bidirectional TVS</b> 12 V / 200 W in SMF/SOD-123FL More see <a href="https://diotec.com/en/productlist/TVS.html">https://diotec.com/en/productlist/TVS.html</a>
<b>MMBT7002DW</b>	<b>Dual N-MOSFET</b> 0.115 A / 60 V in SOT-363 More see <a href="https://diotec.com/en/productlist/FET.html">https://diotec.com/en/productlist/FET.html</a>
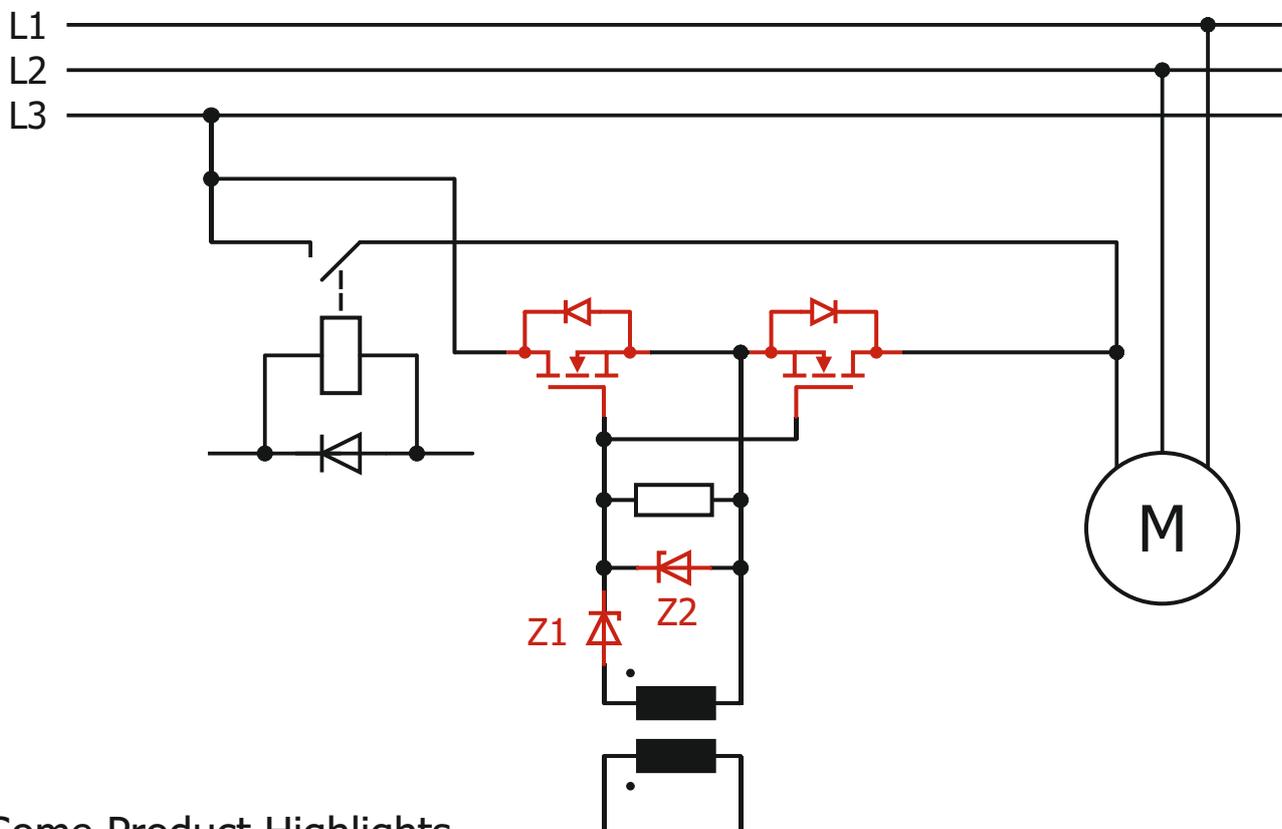
## 7. Softstart realized with MOSFET-based AC Switch

Three phase motors for fans, pumps, conveyor belts and similar are mostly operated at fixed speed. They require a soft start switch for turn-on. It controls the phase angle of just one line and ramps it up slowly. By this, a high starting current and thus mechanical torque is avoided, which leads to a smooth start of the machine and its load. State-of-the art AC switches are thyristors or triacs; in the following, a MOSFET-based solution is introduced.

Two high-voltage MOSFETs connected back-to-back at their Source contacts are operating as an AC switch. The two Gates are driven from the same input, which could be simply realized by a small pulse transformer. A short positive pulse is enough to charge-up the two Gate capacitances. The Zener or ESD protection diode Z1 avoids discharge via the transformer coil at zero output. A negative transformer pulse leads to forward biasing of Z2, which in consequence turns-off the Gates. Pulse voltage must be big enough to drive the Zener or ESD into breakdown without overload. Z2 protects the Gates of the MOSFETs, while the resistor discharges it in the off-state. The MOSFET AC switch is bypassed by a relay during steady-state operation.



### Some Product Highlights

- DI2A2N100D1K** **N-MOSFET** 2.2 A / 1000 V with protected Gate in D-PAK/TO-252AA  
More see <https://diotec.com/en/productlist/FET.html>
- DIJ006N90** **N-MOSFET** 6 A / 900 V isolated ITO-220AB  
More see <https://diotec.com/en/productlist/FET.html>
- ESD5Z12** **ESD Protection** 12 V / 240 W in SOD-523  
More see <https://diotec.com/en/productlist/TVS.html>

**Do not hesitate to contact us for further questions:**

[technicalsupport@diotec.com](mailto:technicalsupport@diotec.com)

### Disclaimer

This application note describes device, assembly, test and calculation proposals and shall not be considered as assured and proven solution for any application. No warranty or guarantee, expressed or implied is made regarding the correctness of calculations, performance or suitability of any device, material, assembly etc.

## All rights reserved

The information presented in our data sheets and other documents is to the best of our knowledge true and accurate. It describes the type of component or application and shall not be considered as assured characteristics. No warranty or guarantee, expressed or implied is made regarding the capacity, delivery, performance or suitability of any product or circuit etc, neither does it convey any license under the patent rights of others.

Diotec reserves the right to make changes without further notice. However, regular updating of all product information is provided on our website <sup>1)</sup>. All Diotec products are sold and shipped subject to our "Standard Terms and Conditions of Business" <sup>2)</sup>. The reproduction of all documents is prohibited without the expressed written permission of Diotec Semiconductor AG's Managing Board.

## Disclaimer

**1.** All products described or contained are designed and intended for use in standard applications, so called commercial/ industrial grade, requiring an ordinary level of reliability.

**2.** Some products are available with the special grades "AEC-Q101 compliant" respectively "AEC-Q101 qualified". These are automotive standards <sup>3)</sup>.

**3.** Customers using these parts in applications requiring a special or specific grade of quality or reliability, such as (but not limited to) life supporting devices or systems, where failure or malfunction of the product may directly affect human life or health, are obliged to validate whether the use in such cases is appropriate.

Diotec does not assume any liability arising out of such applications or uses of its products. Usage in all such cases is on the own and sole risk of the customer.

**4.** Although Diotec continuously enhances the quality and reliability of its products, customers must incorporate sufficient safety measures in their designs, such as redundancy, fire containment, and anti-failure, so that personal injury, fire or environmental damage can be prevented. Diotec excludes explicitly every implied warranty or liability regarding the fitness of the products to any other than standard applications.

**5.** All information described or contained herein are subject to change without notice. Please contact Diotec to obtain the latest information before incorporating Diotec products into any design.

**6.** All information described and contained herein are intended only to enable the buyer to order Diotec's products. The information must not be used for any other purpose.

**7.** In the event that any product described or contained herein falls under the category of strategic products controlled by the German Federal Office of Economics and Export Control, this product must not be exported without obtaining an export license from the German Federal Ministry for Economic Affairs and Climate Action in accordance with the valid laws.

## Alle Rechte vorbehalten

Die Angaben in unseren Datenblättern und sonstigen Dokumenten sind nach bestem Wissen und Gewissen gemacht. Sie dienen jedoch allein der Beschreibung und sind nicht als zugesagte Eigenschaften im Rechts-Sinne zu verstehen. Es wird keine Gewähr bezüglich Liefermöglichkeit, Ausführung oder Einsatzmöglichkeit der Bauelemente übernommen, noch dass die angegebenen Bauelemente, Baugruppen, Schaltungen etc. frei von Schutzrechten sind.

Wir behalten uns Änderungen der aufgeführten Daten ohne vorherige Ankündigung vor. Alle Änderungen werden jedoch regelmäßig auf unserer Internet-Seite veröffentlicht <sup>1)</sup>. Verkauf und Lieferung von Diotec-Produkten erfolgt gemäß unseren "Allgemeinen Geschäftsbedingungen" <sup>2)</sup>. Die Vervielfältigung aller Dokumente ist nur mit schriftlicher Genehmigung des Vorstandes der Diotec Semiconductor AG gestattet.

## Haftungsausschluss

**1.** Alle beschriebenen oder enthaltenen Produkte sind für den Gebrauch in Standardanwendungen mit einem gewöhnlichen Zuverlässigkeitsniveau entworfen und bestimmt, bekannt als kommerziell/industrielle Anwendungen.

**2.** Einige Produkte sind mit den speziellen Qualifikationen „AEC-Q101 konform“ oder „AEC-Q101 qualifiziert“ erhältlich. Dies sind Automotive-Standards <sup>3)</sup>.

**3.** Falls diese Produkte in Anwendungen verwendet werden sollen, die einen besonderen Grad der Qualität oder Zuverlässigkeit erfordern, z. B. (aber nicht begrenzt auf) lebenserhaltende Geräte oder Systeme, bei denen durch Ausfall oder eine Störung des Produktes menschliches Leben oder Gesundheit direkt beeinflusst werden kann, ist der Anwender verpflichtet sicherzustellen, dass der beabsichtigte Gebrauch des vorgesehenen Produktes unbedenklich ist.

Diotec übernimmt keine Haftung die sich aus solchen Anwendungen oder der Verwendung der Produkte ergibt. Der Gebrauch für alle solche Anwendungen erfolgt auf eigenes und ausschließliches Risiko des Anwenders.

**4.** Obwohl Diotec die Qualität und die Zuverlässigkeit seiner Produkte beständig erhöht, müssen Kunden ausreichende Sicherheitsvorkehrungen in ihren Designs vornehmen – wie Redundanz, Feuereindämmung und Ausfallschutz – damit Personenschäden, Feuer oder Umweltschädigung verhindert werden können. Diotec schließt ausdrücklich jede implizierte Garantie oder Verbindlichkeit aus, welche die Eignung der Produkte zu irgendwelchen anderen als Standardanwendungen betrifft.

**5.** Alle Informationen, die hier beschrieben oder enthalten sind, können jederzeit ohne jede Benachrichtigung geändert werden. Vor Einsatz eines Diotec Produktes in irgendeiner Anwendung sind bei Diotec die neuesten Informationen einzuholen.

**6.** Alle Informationen, die hier beschrieben oder enthalten sind, sollen dem Kunden nur ermöglichen, Diotec Produkte zu bestellen. Die Informationen dürfen zu keinem anderen Zweck verwendet werden.

**7.** Sollte ein hier beschriebenes oder enthaltenes Produkt unter Beschränkungen fallen, die durch das deutsche Bundesamt für Wirtschaft und Ausfuhrkontrolle geregelt werden, darf dieses Produkt in Übereinstimmung mit den gültigen Gesetzen nicht ohne Exportgenehmigung vom deutschen Bundesministerium für Wirtschaft und Klimaschutz exportiert werden.

1 Refer to <http://diotec.com/> "Products/Product Changes" respectively "News/Datasheets"  
Siehe <http://diotec.com/> „Produkte/Produktänderungen“ bzw. „News/Datenblätter“

2 Refer data book or <http://diotec.com/> "Company" – Siehe Datenbuch oder <http://diotec.com/> „Unternehmen“

3 Refer to <http://diotec.com/> "Products/Information/Qualification/Commercial Grade and AEC-Q101"  
Siehe <http://diotec.com/> „Produkte/Informationen/Qualifizierung/Standard und AEC-Q101“